

3)

9) We know that average current through C_2 at steady state is zero.

$$V_o = 12V \quad P_o = 24W \Rightarrow I_o = 2A \quad R_o = R = 6\Omega$$

$$V_{in} = 16V \quad P_{in} = 24W \Rightarrow I_{in} = I_{C1, \text{mean}} = 1.5A$$


↓
assumed
all components
are ideal

We know that $V_o = V_s \left(\frac{D}{1-D} \right)$

$$12 = 16 \left(\frac{D}{1-D} \right) \Rightarrow \frac{D}{1-D} = \frac{3}{4} \Rightarrow 4D = 3 \Rightarrow D = \frac{3}{7}$$

We know that $f_{sw} = 50 \text{ kHz}$ then $T = 20\mu s$

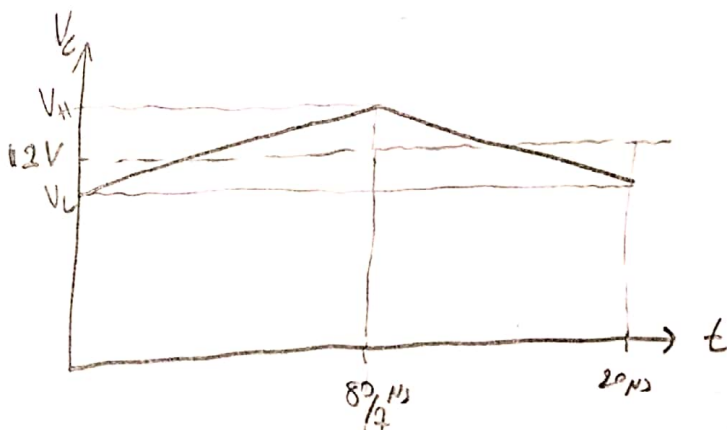While the switch is in conduction \Rightarrow for $\frac{60}{7}\mu s$ capacitor supplies power to the load this means that capacitor is discharging.




switch is not
in conduction
capacitor is
charging

switch in conduction
capacitor is discharging

If we have 2% voltage ripple then

$$V_{H1} = 12.12V, V_L = 11.88V \Rightarrow \Delta V = 0.24V$$

discharging \Rightarrow

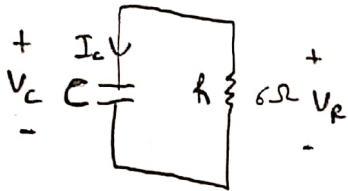

If we assume constant discharging current = 2A then

$$V_C(t) = V_C(0) + \frac{1}{C} \int_0^t i(t) dt$$

$$11.88 = 12.12 + \frac{1}{C} \int_0^{60/4 \mu s} -2 dt$$

$$C = 71.43 \mu F$$

Lets calculate it without assuming constant discharge current. (But for R Load)

$$V_C(t) = V_C(0) + \frac{1}{C} \int_0^t i(t) dt$$

$$i_C = C \frac{dV_C}{dt}$$

$$V_C - V_R = 0 \Rightarrow V_C + C \frac{dV_C}{dt} R = 0 \Rightarrow V_C + CR \dot{V}_C = 0$$

$$+ \frac{1}{CR} V_C + dV_C = 0$$

$$e^{t/CR} dV_C + \left(\frac{1}{CR}\right) e^{t/CR} V_C = 0$$

$$d(e^{t/CR} V_C) = 0$$

$$V_C = C e^{-t/CR}$$

$$V_C(0) = C = 12.12V$$

$$V_C(t) = V_C(0) e^{-t/RC} \Rightarrow V_C\left(\frac{60}{4} \mu s\right) = V_C(0) e^{-\frac{60/4 \mu s}{6C}}$$

$$11.88 = 12.12 e^{-\frac{60/4 \mu s}{6C}}$$

$$-0.02 = -\frac{60/4 \mu s}{6C} \Rightarrow$$

$$C = 71.42 \mu F$$

this shows us that we can use constant discharge current method.